

**Eastern
Economy
Edition**

Network Theory

Analysis and Synthesis

Smarajit Ghosh



Network Theory

Analysis and Synthesis

Smarajit Ghosh

Professor

Department of Electrical and Instrumentation Engineering

Thapar University

Patiala

PHI Learning Private Limited

Delhi-110 092

2015

NETWORK THEORY: Analysis and Synthesis

Smarajit Ghosh

© 2005 by Prentice-Hall of India Private Limited, New Delhi. All rights reserved. No part of this book may be reproduced in any form, by mimeograph or any other means, without permission in writing from the publisher.

ISBN-978-81-203-2638-5

The export rights of this book are vested solely with the publisher.

Ninth Printing

...

...

August, 2015

Published by Asoke K. Ghosh, Prentice-Hall of India Private Limited, M-97, Connaught Circus, New Delhi-110001 and Printed by Mohan Makhijani at Rekha Printers Private Limited, New Delhi-110020.

CONTENTS

Preface

xv

Acknowledgements

xvii

1. Fundamentals of Circuits

1–39

1.1	Charge	1
1.2	Drift Velocity	1
1.3	Current	2
1.4	Current density	2
1.5	Voltage	3
1.6	Energy	3
1.7	Power	3
1.8	Basic Circuit	4
1.9	SI Base Units	4
1.10	Multiples and Submultiples of Units	5
1.11	Some Derived Units	5
1.12	Ohm's Law	5
1.13	Resistance and Resistivity	6
1.14	Conductance and Conductivity	7
1.15	Open Circuit and Short Circuit	8
1.16	Variation of Resistance with Temperature	8
1.17	Variation of Resistivity with Temperature	8
1.18	Conductors, Insulators, Semiconductors, Superconductors	9
1.19	Series Combination of Resistors	9
1.20	Parallel Combination of Resistors	10
1.21	Division of Current in Parallel Resistors	11
1.22	Voltage Division	13
1.23	Inductors	13
1.24	Capacitors	14
1.25	Energy Stored in an Inductor	15
1.26	Energy Stored in a Capacitor	15
1.27	Energy Sources	16
1.28	Source Transformation	18
1.29	Generation of Alternating Voltage	19
1.30	Expression of the Alternating Voltage and Current	20
1.30.1	Representation of E.M.F. Equations	22
1.31	Mean or Average Value of Alternating Current	22

1.32	Root Mean Square (RMS) Value of Alternating Current	23
1.33	Form Factor	26
1.34	Peak/Amplitude/Crest Factor	26
1.35	Signal Waveforms	27
1.35.1	Sinusoidal Signal	27
1.35.2	Exponential Function	27
1.35.3	Unit-Step Function	28
1.35.4	Ramp Function	28
1.35.5	Impulse Function	28
1.35.6	Periodic Function	28
1.36	Additional Solved Examples	29
	<i>Exercises</i>	38

2. Kirchhoff's Laws 40–58

2.1	Basic Definitions	40
2.2	Kirchhoff's Laws	41
2.3	Solving Simultaneous Equations Using Determinants	42
2.4	Nodal Analysis	44
2.5	Maxwell's Loop Current Method	46
2.6	Star–Delta Transformation	47
2.7	Duality	50
2.8	Additional Solved Examples	50
	<i>Exercises</i>	57

3. DC Network Theorems 59–93

3.1	Superposition Theorem	59
3.2	Thévenin's Theorem	60
3.3	Norton's Theorem	62
3.4	Maximum Power Transfer Theorem	64
3.5	Reciprocity Theorem	66
3.6	Millman's Theorem	66
3.7	Substitution Theorem	67
3.8	Compensation Theorem	68
3.9	Tellegen's Theorem	69
3.10	Additional Solved Examples	69
3.11	Circuits Containing Dependent Sources—Numerical Problems	86
	<i>Exercises</i>	92

4. DC Transients 94–111

4.1	RL Circuit	94
4.1.1	Growth of Current	94
4.1.2	Decay of Current	96
4.2	RC Circuit	97
4.2.1	Charging a Capacitor	97
4.2.2	Discharging a Capacitor	99

- 4.3 Transient Response of *RLC* Circuits 101
 4.4 Additional Solved Examples 104
Exercises 110

5. Single-Phase AC Circuits

112–138

- 5.1 Pure Resistive Circuit 112
 5.2 Pure Inductive Circuit 113
 5.3 Pure Capacitive Circuit 113
 5.4 Series *RL* Circuit 114
 5.5 Series *RC* Circuit 116
 5.6 Series *RLC* Circuit 118
 5.7 Parallel *RL* Circuit 120
 5.8 Parallel *RC* Circuit 121
 5.9 Parallel *RLC* Circuit 121
 5.10 Power Relations in AC Circuits 122
 5.11 Power in Pure Resistive Circuits 122
 5.12 Power in Pure Inductive Circuits 123
 5.13 Power in Pure Capacitive Circuits 124
 5.14 Power in a General Series Circuit 125
 5.15 Reactive Power 126
 5.16 Power Triangle 126
 5.17 Complex Power 127
 5.18 Additional Solved Examples 127
Exercises 137

6. Resonance

139–158

- 6.1 Series Resonance 139
 6.1.1 Quality Factor 140
 6.1.2 Sharpness of Resonance 140
 6.1.3 Fractional Detuning Factor (δ) 142
 6.1.4 Expression of Z in Terms of Fractional Detuning Factor δ and Quality Factor Q 142
 6.1.5 Expression for Half-Power Frequencies in *RLC* Series Resonant Circuits 143
 6.1.6 Selectivity 144
 6.1.7 Frequency at which V_C is Maximum 144
 6.1.8 Frequency at which V_L is Maximum 145
 6.1.9 Variation of Z and I with Frequency 146
 6.2 Parallel Resonance 146
 6.2.1 Relationship among Z , δ , Q 148
 6.2.2 Resonance between Parallel *RL* and *RC* Circuits 150
 6.2.3 Parallel *RLC* Circuit 152
 6.3 Additional Solved Examples 152
Exercises 157

7. Three-Phase Systems	159–184
7.1 Advantages of the Three-Phase System	160
7.2 Numbering of Phases	161
7.3 Interconnection of Three-Phases	161
7.3.1 Star and Delta Connections	161
7.4 Voltages, Currents, and Power in Star Connection	162
7.5 Voltages, Currents and Power in Delta Connection	164
7.6 Star-Connected Load	166
7.7 Measurement of Power in Three-Phase Systems	168
7.8 Two Wattmeter Method	169
7.9 Unbalanced Load	171
7.10 Calculation of Neutral Shift	172
7.11 Balanced Delta-Connected Load	172
7.12 Additional Solved Examples	173
<i>Exercises</i>	183
8. Fourier Series and Fourier Transform	185–227
8.1 Fourier Series	185
8.2 Dirichlet Conditions	186
8.3 Orthogonal Functions	186
8.4 Determination of Fourier Coefficients	187
8.5 Wave Symmetry	191
8.5.1 Even or Mirror Symmetry	191
8.5.2 Odd or Rotation Symmetry	192
8.5.3 Half-Wave Symmetry	193
8.5.4 Quarter-Wave Symmetry	194
8.6 Exponential Form of Fourier Series	196
8.7 Fourier Transform	199
8.8 Fourier Transform of Some Functions	201
8.8.1 Fourier Transform of Gate Function	201
8.8.2 Fourier Transform of Impulse Function	202
8.8.3 Fourier Transform of Shifted Impulse Function	203
8.8.4 Fourier Transform of One-Sided Exponential Function	203
8.8.5 Fourier Transform of Two-Sided Exponential Function	204
8.8.6 Fourier Transform of $\text{sgn}(t)e^{-a(t)}$	205
8.8.7 Fourier Transform of Signum Function	206
8.8.8 Fourier Transform of $f(t) = 1$	206
8.8.9 Fourier Transform of $u(t)$	207
8.9 Fourier Transformation Theorems	208
8.9.1 Linearity	208
8.9.2 Time Scaling	208
8.9.3 Time Differentiation	209
8.9.4 Time Shifting Property	210
8.9.5 Translation in the Frequency Domain	210

8.9.6	Modulation Theorem	210
8.9.7	Symmetry or Duality Property	211
8.9.8	Time Convolution Property	211
8.9.9	Frequency Convolution	211
8.9.10	Frequency Differentiation	211
8.9.11	Time Integration	211
8.10	Parseval's Theorem	211
8.11	Additional Solved Examples	212
	<i>Exercises</i>	227

9. Laplace Transform**228–256**

9.1	Laplace Transform	228
9.2	Inverse Laplace Transformation	229
9.3	Basic Properties of Laplace Transforms	229
9.4	Laplace Transform of a Derivative $[df(t)/dt]$	232
9.5	Laplace Transform of an Integral $\int f(t) dt$	233
9.6	Laplace Transform of Some Common Time Functions	233
9.6.1	Unit-Step Function	233
9.6.2	Impulse Function	234
9.6.3	Exponential Function e^{at}	234
9.6.4	Sinusoidal Function	234
9.6.5	Cosine Function	235
9.6.6	Ramp Function	235
9.6.7	Parabolic Function	236
9.6.8	Hyperbolic Sinusoidal Functions	236
9.6.9	Damped Sinusoidal Functions	237
9.6.10	Damped Hyperbolic Sinusoidal Functions	237
9.6.11	Laplace Transform of t^n	238
9.6.12	Laplace Transforms of Some Useful Functions	238
9.7	Initial-Value Theorem	238
9.8	Final-Value Theorem	240
9.9	Partial Fraction Expansion	244
9.10	Relation between Step Response and Impulse Response	247
	<i>Exercises</i>	256

10. Application of Laplace Transform**257–286**

10.1	Resistance Element	257
10.2	Inductance Element	257
10.3	Capacitance Element	258
10.4	Step Response of <i>RL</i> Circuit	259
10.5	Step Response of <i>RC</i> Circuit	260
10.6	Step Response of <i>RLC</i> Circuit	260
10.7	Impulse Response of Series <i>RL</i> Circuit	262
10.8	Impulse Response of Series <i>RC</i> Circuit	263

- 10.9 Pulse Response 263
- 10.10 Pulse Response of Series RC Circuit 264
- Exercises* 285

11. Analysis of Special Signal Waveforms 287–300

- 11.1 Basic Types of Special Signals 287
 - 11.1.1 Shifted Unit-Step Function 287
 - 11.1.2 Ramp Function 288
 - 11.1.3 Impulse Function 289
 - 11.1.4 Unit-Doublet Function 290
- 11.2 Laplace Transformation of Some Special Signal Waveforms 290
 - 11.2.1 Shifted Unit-Step Function 290
 - 11.2.2 Impulse Function 290
 - 11.2.3 Unit-Doublet Function 291
 - 11.2.4 Ramp Function 291
- Exercises* 299

12. Application of Kirchhoff's Laws and Network Theorems to AC Circuits 301–324

- 12.1 Mesh Analysis 301
- 12.2 Nodal Analysis 302
- 12.3 Thévenin's and Norton's Theorems 304
- 12.4 Superposition Theorem 311
- 12.5 Maximum Power Transfer Theorem 314
- 12.6 Millman's Theorem 316
- 12.7 Reciprocity Theorem 317
- 12.8 Additional Solved Examples 318
- Exercises* 323


13. Coupled Circuits 325–345

- 13.1 Self-Inductance 325
- 13.2 Mutual Coupling 327
- 13.3 Magnetic Coupling 327
- 13.4 Mutual Inductance 328
- 13.5 Coefficient of Coupling 328
- 13.6 Dot Convention 331
- 13.7 Inductive Coupling in Series 331
- 13.8 Inductive Coupling in Parallel 334
- 13.9 Tuned Coupled Circuits 336
 - 13.9.1 Single-Tuned Coupled Coils 336
 - 13.9.2 Double-Tuned Coupled Coils 339
- 13.10 Additional Solved Examples 341
- Exercises* 344

14. Two-Port Networks**346–403**

- 14.1 Network Configurations 346
- 14.2 z -Parameters 349
- 14.3 y -Parameters 351
- 14.4 h -Parameters 352
- 14.5 $ABCD$ -Parameters 353
- 14.6 Equivalent Circuit Using z -Parameters 355
- 14.7 Equivalent Circuit Using y -Parameters 356
- 14.8 Equivalent Circuit Using h -Parameters 356
- 14.9 Condition for Reciprocity and Symmetry of Two-Port Networks in Different Parameters Representations 357
 - 14.9.1 Reciprocity and Symmetry in z -Parameter Representation 357
 - 14.9.2 Reciprocity and Symmetry in y -Parameter Representation 358
 - 14.9.3 Reciprocity and Symmetry in h -Parameter Representation 359
 - 14.9.4 Reciprocity and Symmetry in $ABCD$ -Parameter Representation 360
- 14.10 Interrelationships between Parameters of Two-Port Network 361
 - 14.10.1 z -Parameters in Terms of y -Parameters 361
 - 14.10.2 z -Parameters in Terms of h -Parameters 362
 - 14.10.3 z -Parameters in Terms of $ABCD$ -Parameters 363
 - 14.10.4 y -Parameters in Terms of z -Parameters 364
 - 14.10.5 y -Parameters in Terms of h -Parameters 365
 - 14.10.6 y -Parameters in Terms of $ABCD$ -Parameters 365
 - 14.10.7 h -Parameters in Terms of z -Parameters 366
 - 14.10.8 h -Parameters in Terms of y -Parameters 367
 - 14.10.9 h -Parameters in Terms of $ABCD$ -Parameters 367
 - 14.10.10 $ABCD$ -Parameters in Terms of z -Parameters 368
 - 14.10.11 $ABCD$ -Parameters in Terms of y -Parameters 369
 - 14.10.12 $ABCD$ -Parameters in Terms of h -Parameters 370
- 14.11 Interconnection of Two-Port Networks 371
 - 14.11.1 Cascade Connection 371
 - 14.11.2 Series Connection 372
 - 14.11.3 Parallel Connection 373
 - 14.11.4 Series-Parallel Connection of Two-Port Networks 374
- 14.12 Analysis of Typical Two-Port Networks 374
 - 14.12.1 T-Network 375
 - 14.12.2 π -Network 376
 - 14.12.3 Lattice Network 378
- 14.13 Open-Circuit and Short-Circuit Impedances and the $ABCD$ -Parameters 379
- 14.14 Input and Output Impedances of Terminated Two-Port Networks 381
 - 14.14.1 Input Impedance in Terms of z -Parameters 382
 - 14.14.2 Input Impedance in Terms of y -Parameters 382
 - 14.14.3 Input Impedance in Terms of $ABCD$ -Parameters 383
 - 14.14.4 Input Impedance in Terms of h -Parameters 384
 - 14.14.5 Output Impedance in Terms of z -Parameters 384

Network Theory Analysis and Synthesis

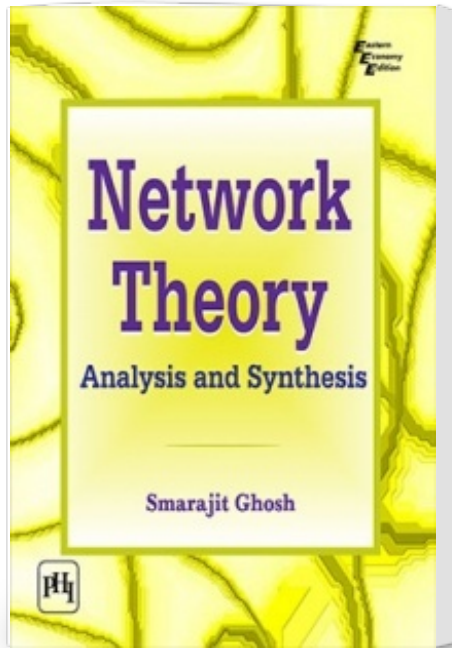

Publisher : PHI Learning

ISBN : 9788120326385

Author : Smarajit Ghosh

Type the URL : <http://www.kopykitab.com/product/6181>



Get this eBook