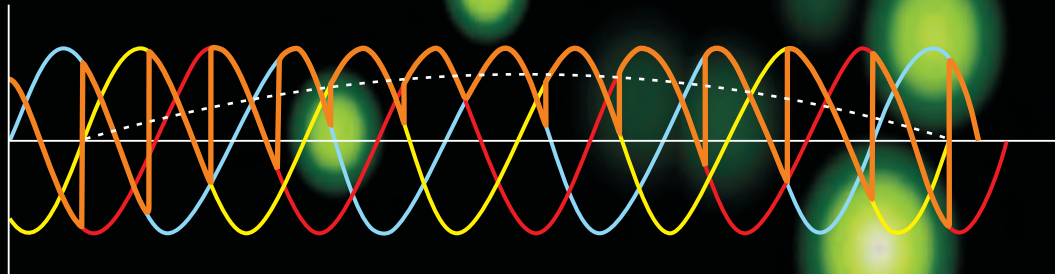


Eastern
Economy
Edition

Second Edition



Power Electronics

Devices and Circuits



V. Jagannathan

Power Electronics

Devices and Circuits

SECOND EDITION

V. Jagannathan

*Professor and Head
Department of Electrical and Electronics Engineering
Coimbatore Institute of Technology
Coimbatore*

PHI Learning Private Limited

New Delhi-110001
2011

POWER ELECTRONICS: Devices and Circuits, Second Edition

V. Jagannathan

© 2011 by PHI Learning Private Limited, New Delhi. All rights reserved. No part of this book may be reproduced in any form, by mimeograph or any other means, without permission in writing from the publisher.

ISBN-978-81-203-4196-8

The export rights of this book are vested solely with the publisher.

Seventh Printing (Second Edition)

...

...

November, 2010

Published by Asoke K. Ghosh, PHI Learning Private Limited, M-97, Connaught Circus, New Delhi-110001 and Printed by Baba Barkha Nath Printers, Bahadurgarh, Haryana-124507.

Contents

Preface

xi

1. Introduction

1–19

- 1.1 What is Power Electronics? 1
- 1.2 History 1
- 1.3 Power Electronics Applications 2
- 1.4 Power Semiconductor Devices and Their Classifications 3
- 1.5 Power Semiconductor Devices: Characteristics and Ratings 5
- 1.6 Ideal and Real Switches: Comparison of Characteristics 7
 - 1.6.1 Ideal Switch Characteristics 7
 - 1.6.2 Desirable Characteristics of a Real Switch 7
 - 1.6.3 Power Loss Characteristics of an Ideal Switch 7
 - 1.6.4 Power Loss Characteristics in a Real Switch 8
- 1.7 Power Electronic Systems 10
- 1.8 Types of Power Electronic Circuits/Converters 11
- 1.9 Merits and Demerits of Power Electronic Converters 12
- 1.10 Recent Developments 12
- Summary 13
- Solved Examples 14
- Review Questions 18
- Problems 18

2. Power Switching Devices and their Characteristics

20–108

- 2.1 Preliminaries 20
- 2.2 Power Diodes 20
 - 2.2.1 Diode V–I Characteristics 21
 - 2.2.2 Diode Reverse Recovery Characteristics 22
 - 2.2.3 Types and Ratings of Power Diodes 22
 - 2.2.4 Series and Parallel Operation of Diodes 23

2.3	Thyristors	24
2.3.1	Structure, Symbol, and V–I Characteristics	24
2.3.2	Transistor Analogy	26
2.3.3	Thyristor Turn-on Methods	27
2.3.4	Thyristor Turn-off Methods	30
2.4	Switching Characteristics of Thyristors	30
2.4.1	Switching Characteristics during Turn-on	30
2.4.2	Switching Characteristics during Turn-off	32
2.5	Thyristor Gate Characteristics	33
2.6	Thyristor Commutation Methods	35
2.6.1	Natural Commutation	35
2.6.2	Forced Commutation	35
2.7	Thyristor Protection	39
2.7.1	Over Voltage Protection	40
2.7.2	Suppression of Overvoltages	40
2.7.3	Overcurrent Protection	41
2.7.4	Snubber Circuits	44
2.8	Thyristor Ratings	44
2.8.1	Anode Voltage Ratings	45
2.8.2	Current Ratings	46
2.8.3	Surge Current Rating	49
2.8.4	I^2t Rating	49
2.8.5	di/dt Rating	50
2.9	Series and Parallel Operation of Thyristors	50
2.9.1	Series Operation	51
2.9.2	Parallel Operation	53
2.10	Triggering of Thyristors	55
2.10.1	Triggering of Thyristors in Series	55
2.10.2	Triggering of Parallel Connected SCRs	57
2.11	Heat Sinks, Heating, Cooling and Mounting of Thyristors	57
2.11.1	Thermal Resistance	58
2.11.2	Thyristor Heat Sinks	59
2.12	Thyristor Trigger Circuits	59
2.12.1	RC Firing Circuits	59
2.12.2	Synchronized UJT Triggering (or Ramp Triggering)	61
2.12.3	Ramp and Pedestal Triggering	62
2.12.4	Pulse Transformers	63
2.13	Other Thyristor Devices	64
2.13.1	TRIAC	64
2.13.2	DIAC	65
2.13.3	LASCRC	66
2.13.4	Programmable Unijunction Transistor (PUT)	67
2.13.5	Silicon Unilateral Switch (SUS)	67
2.13.6	Reverse Conducting Thyristor (RCT)	67
2.13.7	GTO (Gate-Turn-Off) Thyristor	68

2.14	Power Transistors	73
2.14.1	Bipolar Junction Transistor (BJT)	73
2.15	Power MOSFET	78
2.16	Comparison of MOSFET and BJT	82
2.17	Insulated Gate Bipolar Transistor (IGBT)	82
2.17.1	Basic Structure	83
2.17.2	Equivalent Circuit	84
2.17.3	Operation Models	85
2.17.4	Output Characteristics	85
2.17.5	Transfer Characteristics	86
2.17.6	Switching Characteristics	86
2.17.7	Latch-up	87
2.17.8	Safe Operating Area (SOA)	87
2.17.9	Applications	87
2.18	MOS Controlled Thyristor (MCT)	88
2.19	Typical Rating of High Power Devices	88
2.20	Driver Circuits for Gate Commutation Devices	89
2.20.1	GATE Drive Circuits for Power MOSFET	89
2.20.2	Driver Circuits for MOSFET	90
2.20.3	Driver Circuits for IGBT	91
2.20.4	Base-Drive Circuits for Power BJT	92
2.20.5	GATE Drive Circuits for GTO	92
	Solved Examples	93
	Review Questions	104
	Problems	108

3. AC to DC Converters

109–166

3.1	Preliminaries	109
3.2	The Principle of Phase Control	110
3.3	Converter Classifications	113
3.3.1	Single-phase Half Wave Thyristor Rectifier with RL Load	114
3.3.2	Single-phase Half Wave Thyristor Rectifier with RL Load and Free-wheeling Diode	116
3.3.3	Single-phase Half Wave Thyristor Rectifier with RLE Load	117
3.4	Single-phase Full Wave Thyristor Converters	118
3.4.1	Single-phase Full Wave Mid-point Thyristor Converter	118
3.5	Single-phase Full Wave Bridge Converters	120
3.5.1	Single-phase Bridge Rectifier Connected to Resistance Load	120
3.5.2	Series RL Load	121
3.5.3	RL Load with Free-wheeling Diode	122
3.6	Full Wave Bridge Rectifier Feeding RLE Load	122
3.7	Single-phase Semi-converter	124
3.8	Calculation of Active and Reactive Power Inputs	125
3.9	Effect of Load Inductance	127
3.10	Three-phase Thyristor Converter Circuits	127
3.10.1	Three-phase Half Wave Converter	128

3.10.2	Three-phase Full Converters	129
3.10.3	Line Commutated Three-phase Inverter	133
3.10.4	Three-phase Semi-converters	134
3.11	Effect of Source Impedance on the Performance of Converters	135
3.11.1	Single-phase Full Converter	136
3.11.2	Three-phase Full Converter Bridge	138
3.12	Dual Converters	139
3.12.1	Dual Converter without Circulating Current	141
3.12.2	Dual Converter with Circulating Current	141
3.13	Single Phase Series Converters	142
3.13.1	Two Semiconverters in Series	142
3.13.2	Two Single Phase Full Converters in Series	144
3.13.3	Twelve-pulse Converters	146
3.14	Gating Circuits	147
3.15	Cosine Firing Scheme	147
	Solved Examples	149
	Review Questions	161
	Problems	164

4. AC to AC Converters

167–196

4.1	Preliminaries	167
4.2	AC Voltage Controllers	167
4.2.1	Types of AC Voltage Controllers	168
4.3	Methods of Voltage Control	170
4.3.1	Single-phase AC Voltage Controller Supplying R Loads (Phase Control)	170
4.3.2	Single-phase AC Voltage Controller Supplying R Loads (Integral Cycle Control)	172
4.4	Single-phase Voltage Controller Supplying RL Loads	173
4.5	Three-phase AC Voltage Controller	176
4.6	Single-phase Transformer Tap Changer	178
4.7	Cycloconverters	180
4.7.1	Principle of Operation	181
4.7.2	Single-phase to Single-phase Cycloconverter Feeding RL Load	183
4.7.3	Three-phase to Single-phase Cycloconverters	184
4.7.4	Three-phase to Three-phase Cycloconverter	187
4.8	Output Voltage Equation	188
4.9	Effect of Source Inductance	189
	Solved Examples	190
	Review Questions	194
	Problems	195

5. DC to DC Converters (Choppers)

197–248

5.1	Preliminaries	197
5.2	Principle of Chopper Operation	197

5.3	Control Schemes	199
5.3.1	Constant Frequency Scheme	199
5.3.2	Variable Frequency Scheme	199
5.3.3	Current Limit Control (CLC)	200
5.4	Step Up Choppers	200
5.5	Chopper Circuits: Classification	202
5.6	Steady State Time–Domain Analysis of Type A Chopper	206
5.7	Thyristor Based Chopper Circuits	208
5.7.1	Voltage Commutated Chopper	209
5.7.2	Current Commutated Chopper	212
5.7.3	Load Commutated Chopper	214
5.8	Multiphase Choppers	215
5.9	Switch Mode Power Supplies (SMPS)	217
5.10	Switch Mode DC–DC Converter (without Isolation)	218
5.10.1	Buck Converter	218
5.10.2	Boost-type Converter	220
5.10.3	Buck Boost Converter	223
5.10.4	Cuk Converters	225
5.11	Switch Mode DC–DC Converter (with Isolation)	225
5.11.1	Fly Back Converter	226
5.11.2	Push–Pull Converter	227
5.11.3	Half-bridge Converter	228
5.11.4	Full-bridge Converter	229
5.12	Resonant Converters	230
5.12.1	Zero-current Switching Resonant Converters	231
5.12.2	Zero-voltage Switching Resonant Converters	236
5.12.3	Comparison between ZCS and ZVS converters	240
	Solved Examples	241
	Review Questions	246
	Problems	247

6. Inverters

249–298

6.1	Preliminaries	249
6.2	Classification	249
6.3	Parallel Inverters	250
6.3.1	Basic Parallel Inverter	250
6.3.2	Modified Parallel Inverter	252
6.4	Series Inverters	253
6.4.1	Basic Series Inverter	253
6.4.2	Modifications of Series Inverter	255
6.5	Single-phase Bridge Voltage Source Inverter	256
6.5.1	Single-phase Half Bridge Inverter	256
6.5.2	Single-phase Full Bridge Inverter	259
6.5.3	Steady State Response of Single-phase Inverters	260

6.6	Force Commutated Thyristor Inverter	261
6.6.1	McMurray Inverter (Auxiliary Commutated Inverter)	261
6.6.2	Modified McMurray Full Bridge Inverter	263
6.6.3	McMurray–Bedford Half Bridge Inverter (Complementary Impulse Commutated Inverter)	264
6.7	Three-phase Bridge Inverters	267
6.7.1	Three-phase Inverter under 180° Mode Operation	268
6.7.2	Three-phase Inverter under 120° Mode Operation	271
6.8	Voltage Control in Single-phase Inverters	274
6.8.1	External Control of the AC Output Voltage	274
6.8.2	External Control of the DC Input Voltage Through Variable DC Link	275
6.8.3	Internal Control of the Inverter Voltage	276
6.8.4	Pulse Width Modulated Inverters	277
6.9	Voltage Control of Three-phase Inverter	281
6.10	Harmonic Reduction in the Output Voltage	282
6.10.1	Harmonic Reduction by Transformer Connections	282
6.10.2	Harmonic Reduction by Multiple Commutation in Each Half Cycle	284
6.11	Current Source Inverter	286
6.11.1	Single-phase Capacitor Commutated Current Source Inverter with R Load	286
6.11.2	Single-phase Auto-sequential Commutated Inverter (One-phase ASCI)	287
6.12	Three-phase Current Source Inverter	288
	Solved Examples	289
	Review Questions	296
	Problems	298

7. Power Controllers: Their Applications

299–334


7.1	Preliminaries	299
7.2	DC Motor Speed Control	299
7.2.1	Principle of Speed Control	300
7.3	Phase Controlled Converters	301
7.3.1	Single-phase DC Drives	303
7.3.2	Three-phase DC Drives	308
7.3.3	Dual Converter Drives	311
7.4	Chopper Controlled DC Drives	312
7.5	AC Drives	315
7.5.1	Induction Motor Drives	315
7.5.2	Speed Control by Stator Voltage Control	316
7.5.3	Variable Voltage Variable Frequency Control	317
7.5.4	Speed Control by Chopper Controlled Rotor Resistance	318
7.5.5	Slip Power Recovery Control	319
7.6	Synchronous Motor Control	320
7.7	Static Circuit Breakers	320
7.7.1	DC Circuit Breakers	321
7.7.2	AC Circuit Breakers	321

7.8	HVDC Transmission	322
7.8.1	Types of HVDC Lines	323
7.8.2	Converter Station	324
7.9	Static Var Systems	325
7.9.1	Thyristor Controlled Reactor-fixed (TCR) Capacitor	326
7.9.2	Thyristor Switched Capacitor–Thyristor Controlled Reactor (TSC–TCR)	326
7.10	Uninterrupted Power Supply (UPS)	327
7.10.1	On-Line UPS	327
7.10.2	Off-Line UPS	329
7.10.3	Salient Features of an On-Line Inverter	330
7.10.4	Inverters	331
7.10.5	Transfer Switch	331
	Solved Examples	332
	Review Questions	334

8. Microcontroller Based Control and Protection Circuits **335–364**

8.1	Preliminaries	335
8.2	The 8051 Microcontroller	336
8.2.1	The 8051 Pin Configuration	337
8.2.2	8051 Architecture	339
8.2.3	Memory Organization	339
8.2.4	The Special Function Register	340
8.2.5	Timers/Counters	341
8.2.6	The Serial Interface	341
8.2.7	The Interrupts	341
8.2.8	The Power Control Register (PCON)	342
8.3	The Instruction Set	342
8.3.1	Addressing Modes	342
8.3.2	Arithmetic Instructions	343
8.3.3	Logical Instructions	343
8.3.4	Data Transfer Instructions	344
8.3.5	Boolean Instructions	345
8.3.6	The Program Branching and Machine Control Instructions	345
8.3.7	Instruction Timing	346
8.4	Interfacing the 8051 Microcontroller	346
8.4.1	Interfacing External Memory	346
8.4.2	Interfacing an Input/Output Device	347
8.4.3	Interfacing an Analog to Digital Converter	348
8.4.4	Interfacing a Digital to Analog Converter	349
8.4.5	Interfacing a Relay and an Optocoupler	349
8.4.6	Interfacing a Pulse Transformer	351
8.5	Applications	352
8.5.1	SCR Triggering	352
8.5.2	Cycloconverter	354
8.5.3	Fault Diagnosis in Three-phase Thyristor Converters Using Microcontroller	357

Power Electronics : Devices And Circuits

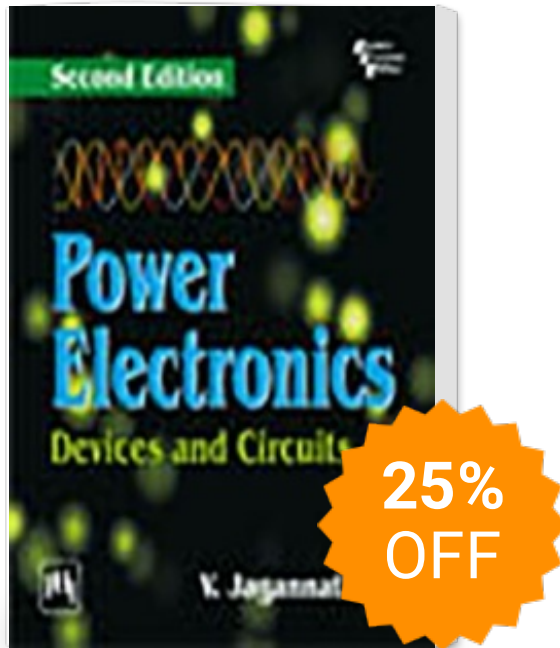

Publisher : PHI Learning

ISBN : 9788120341968

Author : JAGANNATHAN,
V.

Type the URL : <http://www.kopykitab.com/product/7469>



Get this eBook